


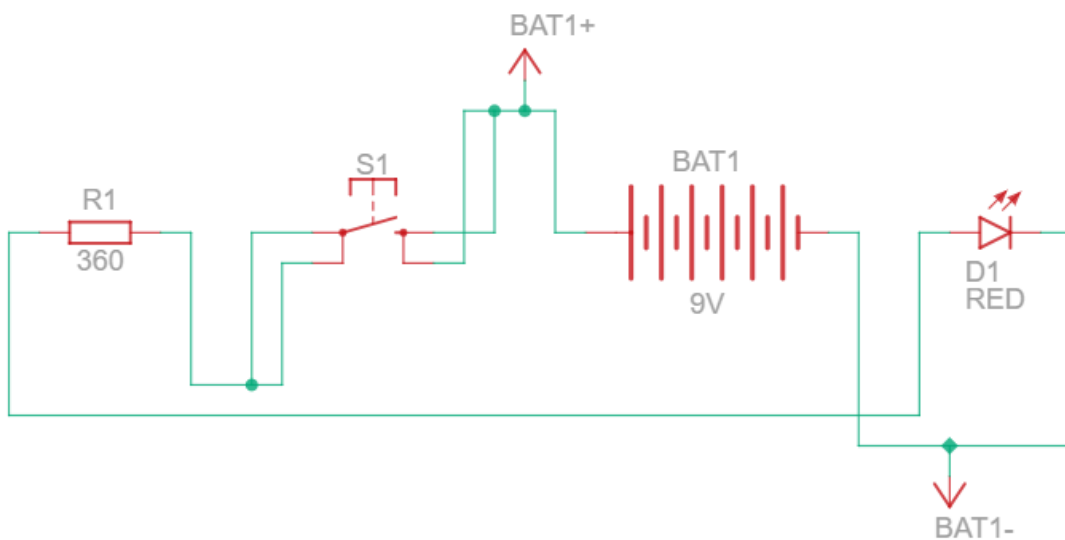
Task 1 - Controlling LED using single Push Button

Aim: Create an electrical circuit to control an LED using a push button.


Component List:

Component List			 Download CSV
Name	Quantity	Component	
BAT1	1	9V Battery	
S1	1	Pushbutton	
D1	1	Red LED	
R1	1	360 Ω Resistor	


Schematic View :



Simulation: (using TINKERCAD)

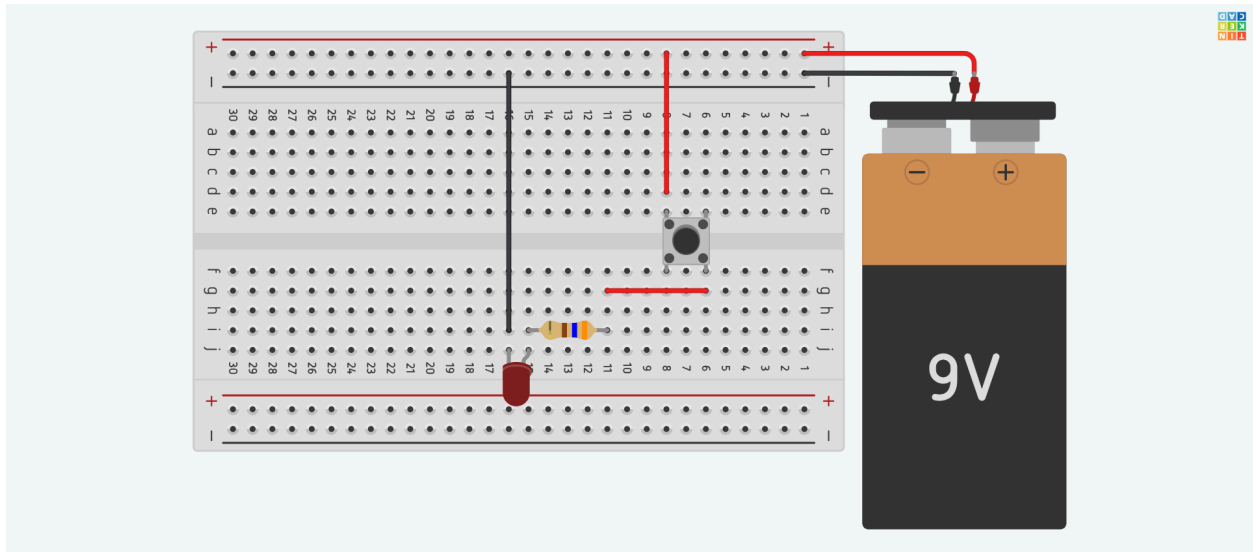


Hands-on experience:

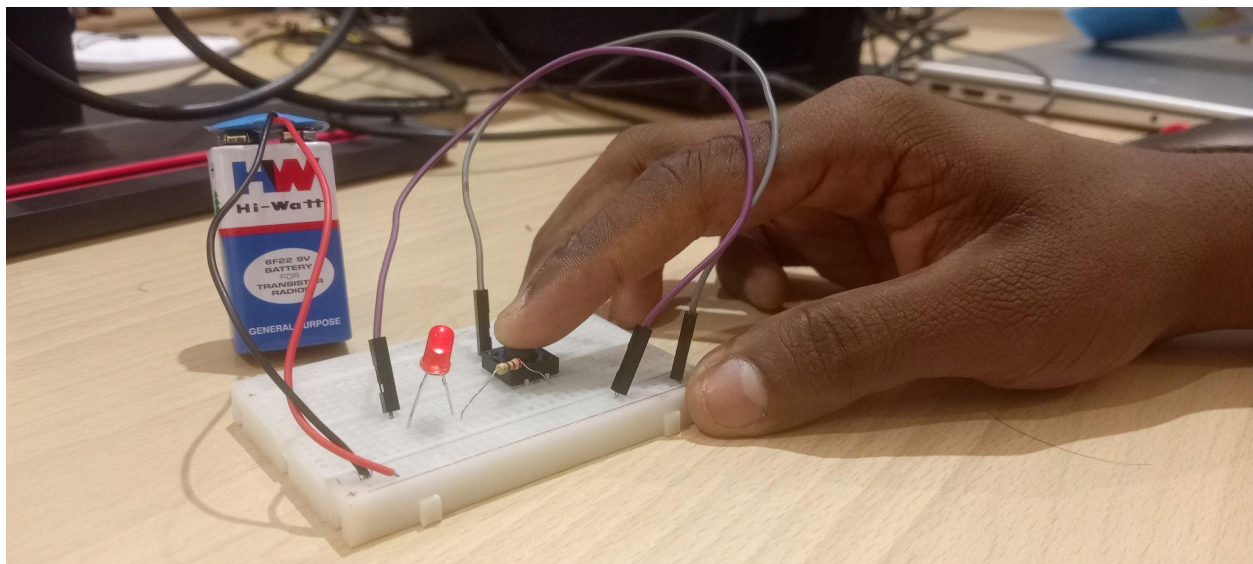


Task 2 - Controlling LED using two Push Button (AND Gate Condition)

Aim: Create an electrical circuit to control an LED using two push buttons, where the LED turns on only when both push buttons are pressed simultaneously (AND gate condition).


Component List:

Component List			 Download CSV
Name	Quantity	Component	
BAT1	1	9V Battery	
S1 S2	2	Pushbutton	
D1	1	Red LED	
R1	1	360 Ω Resistor	


Schematic View :

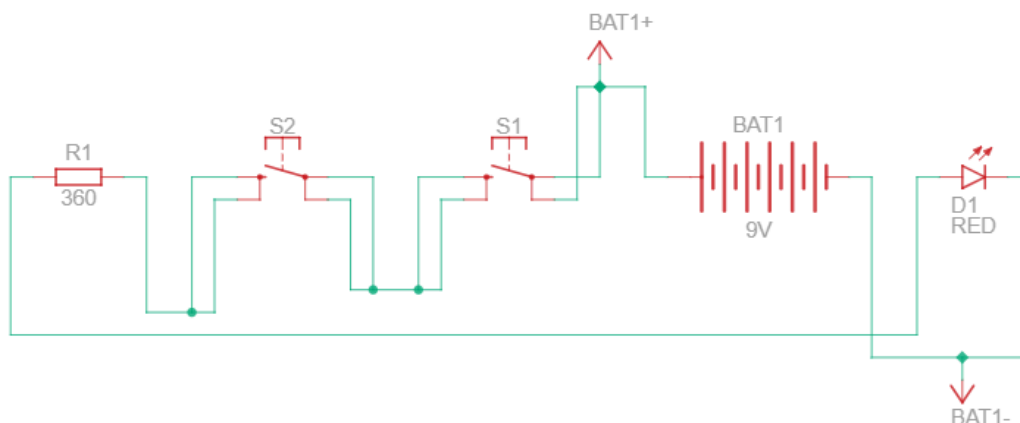

Simulation: (using TINKERCAD)

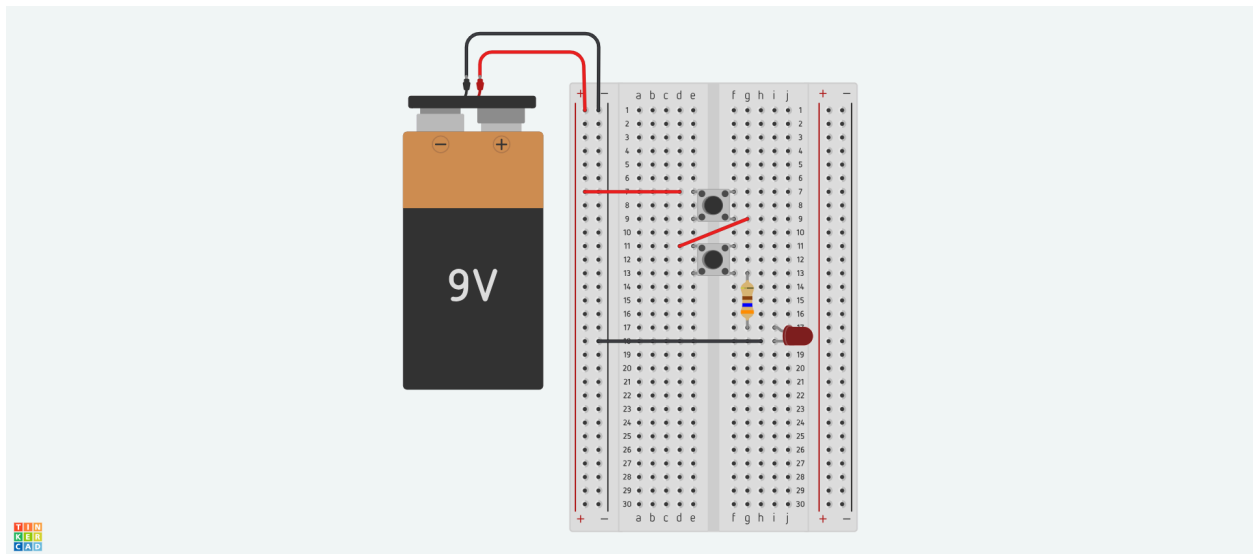


Hands-on experience:

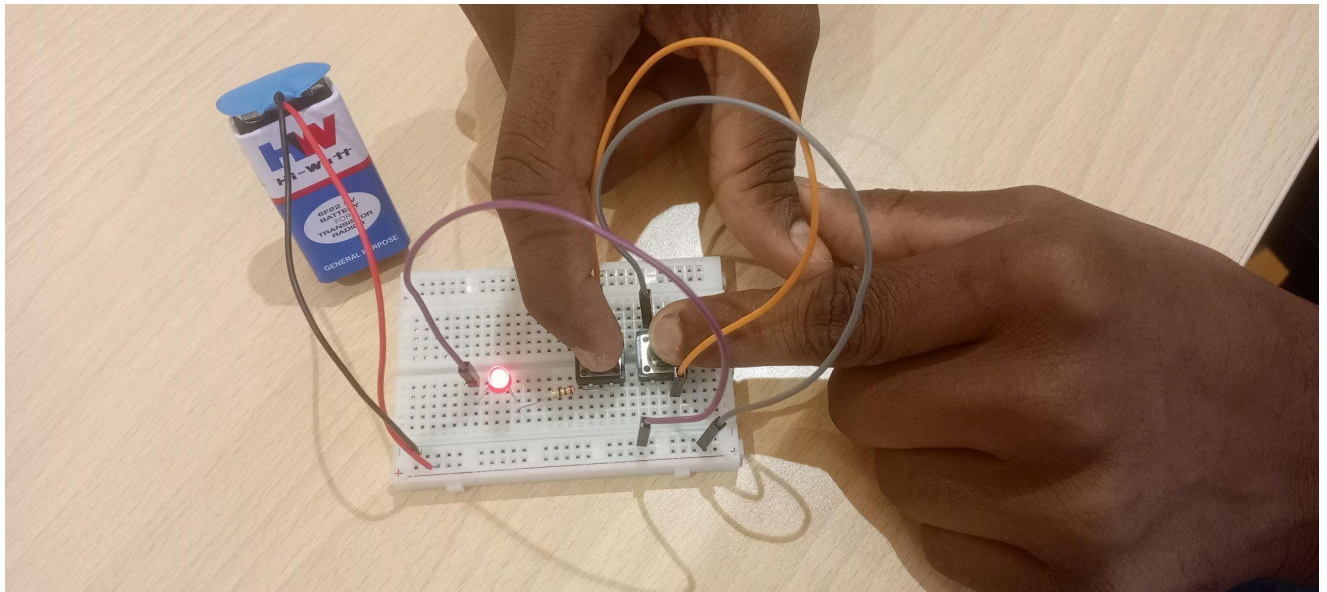


Task 3 - Controlling LED using two Push Button (OR Gate Condition)

Aim: Create an electrical circuit to control an LED using two push buttons, where the LED turns on when either one of the push buttons is pressed (OR gate condition).


Component List:

Component List			 Download CSV
Name	Quantity	Component	
BAT1	1	9V Battery	
S1 S2	2	Pushbutton	
R1	1	360 Ω Resistor	
D1	1	Red LED	


Schematic View :

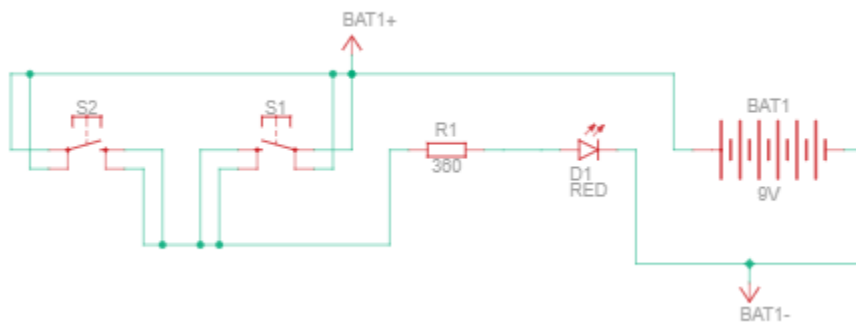

Simulation: (using TINKERCAD)

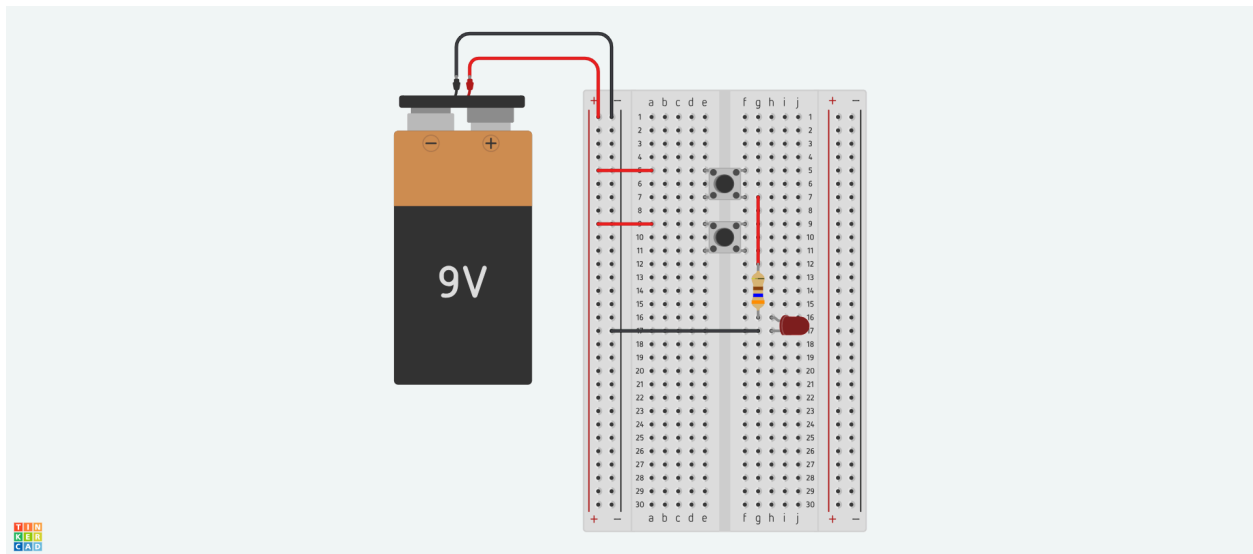

Hands-on experience:

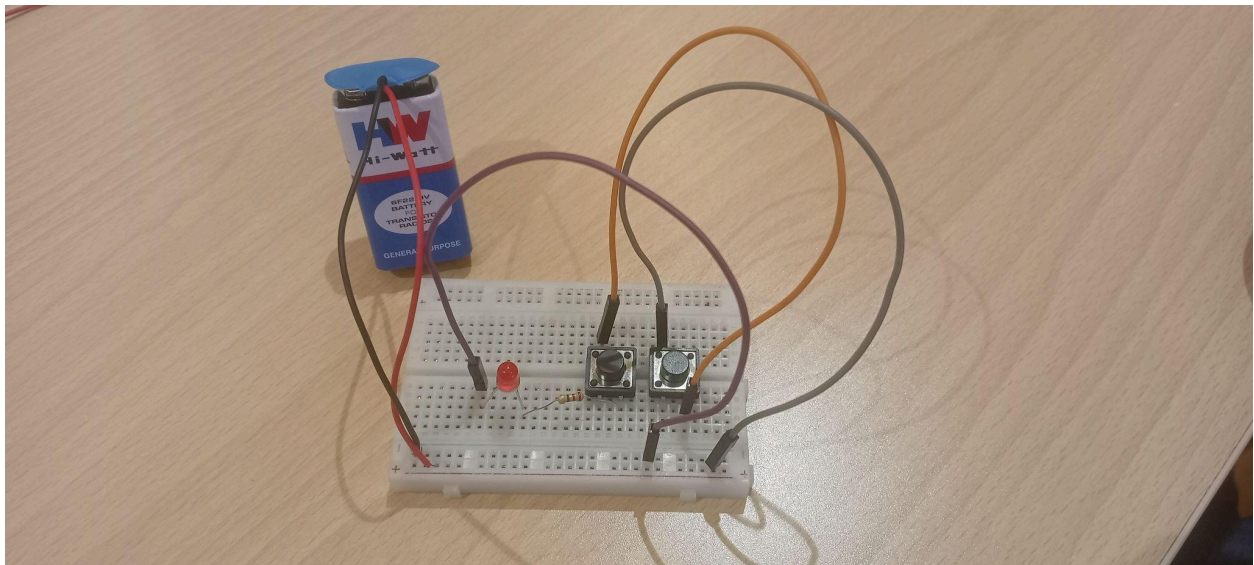

By

1.ANANDHAKUMAR A - anandhakumar.3.3@protosem.tech

2.POOVARASAN K - poovarasan.3.3@protosem.tech